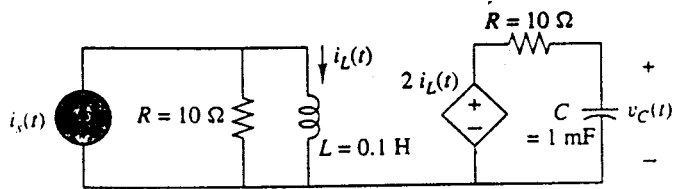


**Problem 1:**

Compute the steady state voltage  $v_c(t)$  across the capacitor for the circuit below when the current through the current source is given by:  $i_s(t) = \cos(100t)A$ .



$$\omega = 100 \frac{\text{rad}}{\text{s}}$$

$$\omega L = 10 \Omega$$

$$\underline{I}_L = \frac{R}{R + j\omega L} \underline{I}_s = \frac{10}{10 + j10} \underline{I}_s$$

$$\underline{I}_s = (1 \angle 0^\circ) A$$

$$= \frac{1}{1 + j} \underline{I}_s = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$\underline{V}_c = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} (2 \underline{I}_L)$$

$$\frac{1}{\omega C} = \frac{1}{10^2 \times 10^{-3}} = 10 \Omega$$

$$= \frac{-j10}{10 - j10} \frac{2}{\sqrt{2}} \angle -45^\circ$$

$$= \frac{1}{1 + j} \frac{2}{\sqrt{2}} \angle -45^\circ = \left( \frac{1}{\sqrt{2}} \angle -45^\circ \right) \left( \frac{2}{\sqrt{2}} \angle -45^\circ \right)$$

$$\underline{V}_c = (1 \angle -90^\circ) V$$

$$\rightarrow v_c(t) = \cos(100t - 90^\circ) V = \sin(100t) V$$

