

## Q #1 (25 pts)

## Laplace

Given ...

$$f(t) = 5 e^{-3t} \cos(4t) u(t), \text{ and}$$

$$g(t) = \int_0^t f(\tau) d\tau + f(t)$$

Derive  $g(t)$  using Laplace techniques.

$$F(s) = \frac{5(s+3)}{(s+3)^2 + 16} = \frac{5s + 15}{s^2 + 6s + 25}$$

$$G(s) = \frac{F(s)}{s} + F(s) = \frac{5s + 15}{s(s^2 + 6s + 25)} + \frac{5s + 15}{s^2 + 6s + 25}$$

$$G(s) = \frac{5s + 15 + 5s^2 + 15s}{s(s^2 + 6s + 25)} = \frac{5s^2 + 20s + 15}{s(s^2 + 6s + 25)}$$

$$G(s) = \frac{A}{s} + \frac{Bs + C}{s^2 + 6s + 25}$$

$$A = sG(s=0) = \frac{15}{25} = 0.6$$

To Find B &amp; C, clear fractions &amp; equate powers of s.

$$5s^2 + 20s + 15 = 0.6s^2 + 3.2s + 15 + Bs^2 + Cs$$

$$s^2: 5 = 0.6 + B \rightarrow B = 4.4$$

$$s^1: 20 = 3.2 + C \rightarrow C = 16.4$$

$$s^0: 15 = 15 \quad \checkmark$$

$$G(s) = \frac{0.6}{s} + \frac{4.4s + 16.4}{s^2 + 6s + 25} = \frac{0.6}{s} + \frac{4.4(s+3)}{(s+3)^2 + 4^2} + \frac{0.8(4)}{(s+3)^2 + 4^2}$$


$$g(t) = (0.6 + 4.4 e^{-3t} \cos 4t + 0.8 e^{-3t} \sin 4t) u(t)$$

Q #2 (25 pts)


Laplace Circuit Analysis

The circuit shown has been in steady state for a long time before the switch opens at  $t=0$ .

Find  $v_1(t)$  using Laplace methods.

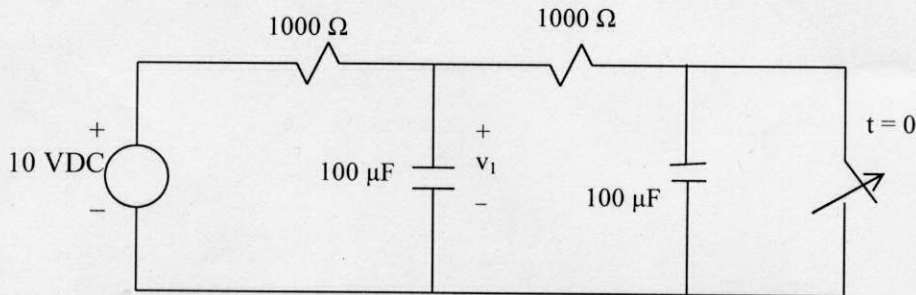

$$v_1(0^-) = 5 \text{ V}$$

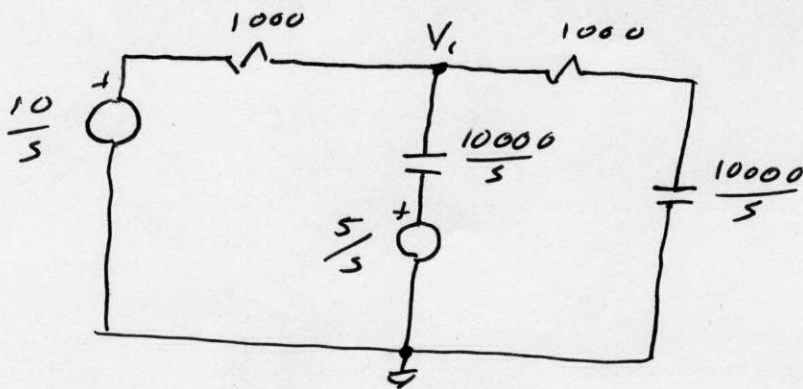

KCL @  $v_1$

$$\frac{v_1 - 10/s}{1000} + \frac{v_1 - 5/s}{10000/s} + \frac{v_1}{1000 + 10000/s} = 0$$

$$v_1 \left( \frac{1}{1000} + \frac{s}{10000} + \frac{1}{1000 + 10000/s} \right) = \frac{1}{100s} + \frac{1}{2000}$$

$$v_1 \left( 1 + \frac{10}{s} + \frac{s}{10} + 1 + 1 \right) = \frac{10}{s} + \frac{100}{s^2} + \frac{1}{2} + \frac{5}{s}$$

$$v_1 = \frac{0.5 + 15/s + 100/s^2}{s/10 + 3 + 10/s} = \frac{0.5s^2 + 15s + 100}{s(0.1s^2 + 3s + 10)}$$

Calculation page

$$V_i = \frac{0.5s^2 + 15s + 100}{s(0.1s^2)}$$

$$V_i = \frac{5s^2 + 150s + 1000}{s(s^2 + 30s + 100)} = \frac{5s^2 + 150s + 1000}{s(s + 3.82)(s + 26.2)}$$

$$V_i = \frac{A}{s} + \frac{B}{s + 3.82} + \frac{C}{s + 26.2}$$

$$A = sV_i(0) = \frac{1000}{(3.82)(26.2)} = 9.99 \text{ V}$$

$$B = (s + 3.82)V_i(-3.82) = \frac{72.964 - 573 + 1000}{(-3.82)(22.38)}$$

$$B = -5.85$$

$$C = (s + 26.2)V_i(-26.2) = \frac{3432 - 3950 + 1000}{(-26.2)(-22.38)}$$

$$C = 0.856$$

$$V_i = \frac{9.99}{s} + \frac{-5.85}{s + 3.82} + \frac{0.856}{s + 26.2}$$


$$v_i(t) = (9.99 - 5.85e^{-3.82t} + 0.856e^{-26.2t}) u(t)$$

Q #3 (25 pts)

Filters

a. Derive the transfer function of this circuit.

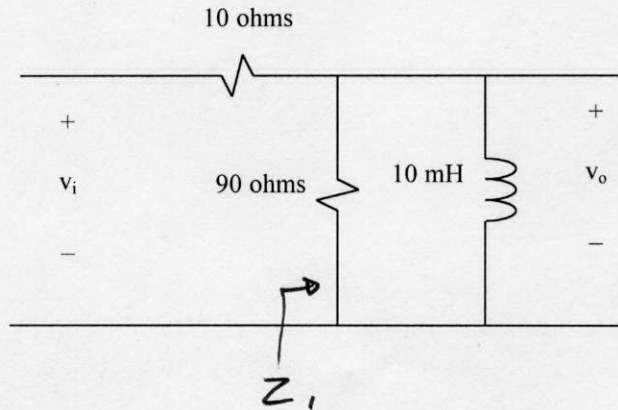
b. Plot the Bode diagram of this transfer function (straight line approximation, magnitude only).



$$Z_1 = 90 \parallel 0.01s = \frac{0.9s}{0.01s + 90} = \frac{90s}{s + 9000}$$

$$H = \frac{Z_1}{Z_1 + 10} = \frac{90s}{(s + 9000) \left( \frac{90s}{s + 9000} + 10 \right)} = \frac{90s}{90s + 10s + 90000}$$
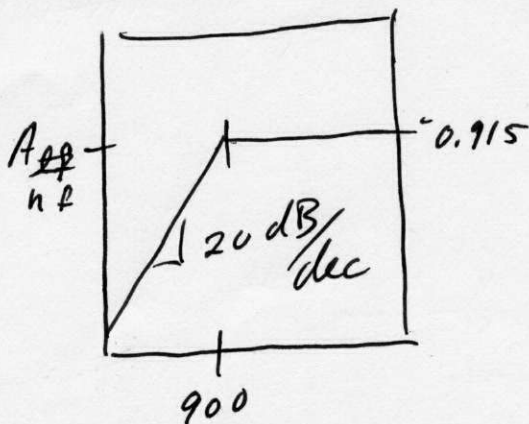
$$H = \frac{90s}{100s + 90000} = \frac{0.9s}{s + 900}$$



$$A_{\text{dB}} = 0.9 = -0.915\ \text{dB}$$

**Q #4 (25 pts)**

**Filters**


Using 100  $\mu$ F capacitors, design a band-pass filter and a band-reject filter, both with the following specifications.

Center frequency: 1000 radians/second

Bandwidth: 100 radians/second

Unity gain at the center frequency

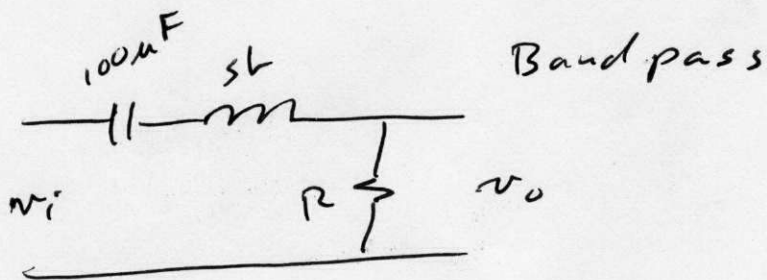**Draw the circuits and specify the component values.**



$$R = 152$$
$$L = 10 \text{ mH}$$

