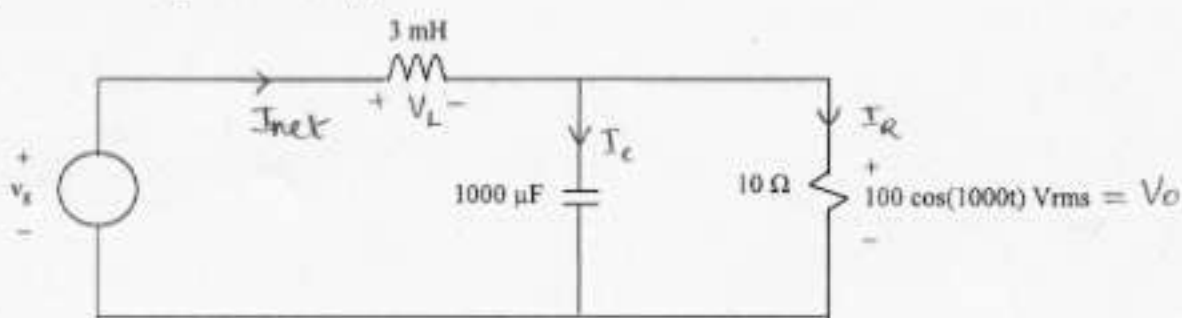


Q #1 (25 pts)

Phasors

Use phasor techniques to find $v_g(t)$.



$$\omega = 1000 \text{ rps}$$

$$V_g = V_L + V_o$$

$$Z_L = j\omega L = j3 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{1000 \times 10^{-6} \times 1000} = -j \Omega$$

$$I_R = \frac{V_o}{R} = \frac{100}{10} = 10 \text{ A}$$


$$I_C = \frac{V_o}{Z_C} = \frac{100}{-j} = j100 \text{ A} = 100 \angle 90^\circ \text{ A}$$

$$I_{net} = I_R + I_C = 10 + j100 = 100.5 \angle 84.28^\circ \text{ A}$$

$$V_L = (I_{net}) j3 \Omega = (10 + j100) j3 = j30 - 300 = 301.5 \angle 174.28^\circ$$

$$V_g = V_L + V_o = 100 + j30 - 300 = -200 + j30 = 202.23 \angle 171.46^\circ$$
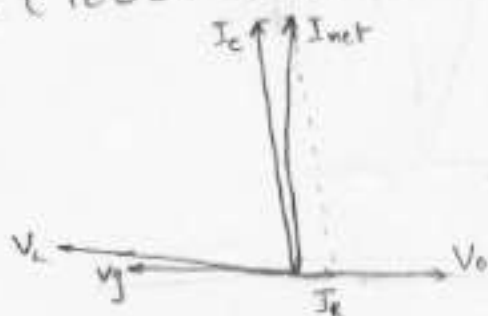
$$V_g = 202.23 \cos(1000t + 171.46^\circ)$$



Q #2 (25 pts)

Phasors

V_g is sinusoidal. The following questions refer to sinusoidal steady-state operation.


a) At what frequency (ω) is V_o zero?

As ω approaches zero or infinity, the ratio V_o/V_g approaches specific values.

b) What value does V_o/V_g approach as ω approaches zero?

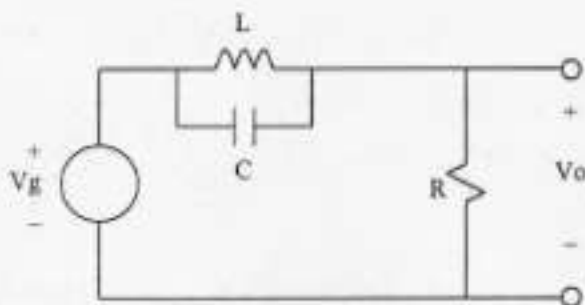c) What value does V_o/V_g approach as ω approaches infinity?

Express your answers in terms of R , L , and C .



$$Z_{net} = R + \frac{j\omega L - \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$

$$= R + \frac{j\omega L}{1 - \omega^2 LC}$$

$$= \frac{R(1 - \omega^2 LC) + j\omega L}{1 - \omega^2 LC}$$

a) $\frac{\bar{V}_o}{\bar{V}_g} = \frac{R}{R + Z_L || Z_C}$; $Z_L || Z_C = \frac{-X_L X_C}{j(X_L + X_C)}$

$\frac{\bar{V}_o}{\bar{V}_g} = \frac{R}{R + \frac{-X_L X_C}{j(X_L + X_C)}} = \frac{j R (X_L + X_C)}{-X_L X_C + j R (X_L + X_C)}$; $\bar{V}_o = 0$ when $X_L + X_C = 0$
ie $\omega L = \frac{1}{\omega C}$; $\therefore \omega = \frac{1}{\sqrt{LC}}$

b) $\frac{V_o}{V_g} = \frac{R}{R + (Z_L || Z_C)} = \frac{R}{R + \frac{j\omega L - \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}} = \frac{R}{R + \frac{j\omega L}{- \omega^2 LC + 1}} = \frac{R(1 - \omega^2 LC)}{j\omega L + R(1 - \omega^2 LC)}$

When $\omega \rightarrow 0$, $\frac{V_o}{V_g} = 1$

c) When $\omega \rightarrow \infty$, by using d'Hopital identity and taking $\lim_{\omega \rightarrow \infty}$

$$\lim_{\omega \rightarrow \infty} \left\{ \frac{R(1 - \omega^2 LC)}{\frac{j\omega L}{- \omega^2 LC + 1} + R(1 - \omega^2 LC)} \right\} = \frac{R(-LC)}{R(-LC)} = 1$$

$\therefore \frac{V_o}{V_g} = 1$


Q #3 (25 pts)

Power

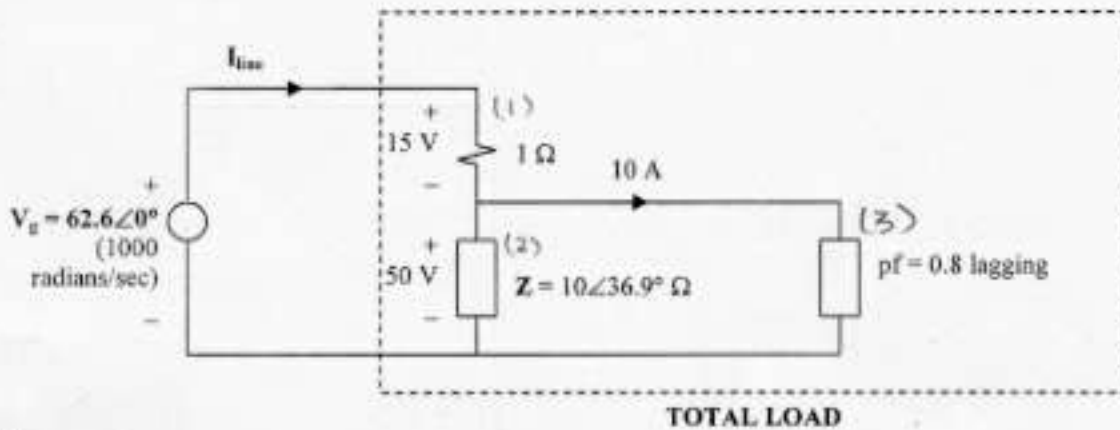- a) Find the power factor of the total load.
- b) Find the phasor value I_{line} (magnitude and angle).
- c) Find the equivalent impedance of the total load.

[All voltages and currents are rms values]

[Unless specified, the phasor angles of the given voltages and currents are not known and should not be assumed to be zero]



$$V_1 = 15V$$

$$Z_1 = 1\Omega$$

$$\therefore P_1 = \frac{V_1^2}{Z_1} = 225W$$

$$V_2 = 50V$$

$$Z_2 = 10 \angle 36.9^\circ$$

$$= 7.996 + j6.0$$

$$S_2 = \frac{V_2^2}{Z_2^*} = \frac{50^2}{7.996 - j6}$$

$$= 200 + j150$$

$$= 250 \angle 36.88^\circ$$

$$\therefore P_2 = 200W$$


$$Q_2 = +150VAR$$

$$V_3 = 50V$$

$$PF = 0.8 \text{ lagging}$$

$$I_3 = 10A$$

$$S_3 = V_3 \cdot I_3 = 500VA$$

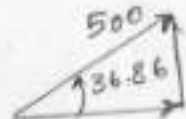


$$P_3 = 400W$$

$$Q_3 = 300VAR$$

$$\therefore P_{net} = P_1 + P_2 + P_3 = 225 + 200 + 400 = 825W$$
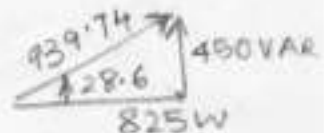
$$Q_{net} = Q_2 + Q_3 = 300 + 150 = 450VAR$$



$$PF = \frac{825}{939.74} = 0.8778 \text{ lagging}$$

$$I_{line} = \frac{939.74}{62.6} = 15.01 \angle 28.6^\circ$$

Calculation page

↳ Equivalent impedance of the load:

$$S_{net} = P_{net} + j Q_{net} = 825 + j450 = 939.74 \angle 28.6^\circ \text{ VA}$$

$$Z_{net} = \frac{S_{net}}{I_{line}^2} = \frac{939.74 \angle 28.6}{15.01^2}$$

$$= 4.171 \angle 28.6^\circ$$

Q #4 (25 pts)

Power

Two loads are attached to a 60 Hz (377 radians/sec), 480 Vrms source.

Load 1: 5 kW, pf: 0.6 lagging

Load 2: 3 kVA, pf: 0.9 leading


Your job is to boost the power factor of the combined load to 0.9.

a) What is the original power factor of the combined load (load 1 and load 2 together)?

b) How would you increase the combined power factor to 0.9?

Be specific - What would you use? Where would you put it? Values?


Load 1:

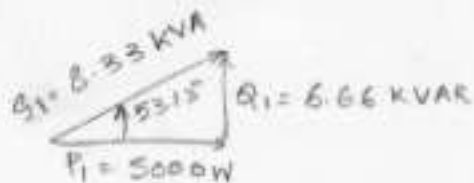

$$\theta = \cos^{-1} 0.6$$

$$= 53.13^\circ$$

Load 2:

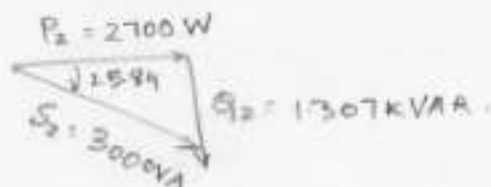

$$\theta = \cos^{-1} 0.9$$

$$= 25.84^\circ$$




a) pf of combined load:

$$pf = \frac{7.7 \times 10^3}{9.377 \times 10^3} = 0.821$$

$$\theta = 34.799^\circ$$

(b)

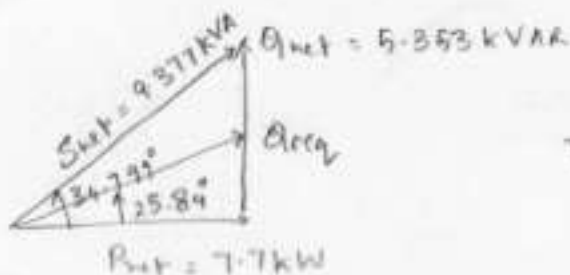

To increase pf = 0.9,

$$\theta_{new} = 25.84^\circ$$

$$\Delta Q = 5353 - 7700 \tan 25.84^\circ = 1623.7 \text{ VAR}$$

$$1623.7 = \frac{V^2}{X_c} = WC V^2$$

$$\therefore C = \frac{1623.7}{480^2 \times 377} = 18.69 \mu\text{F}$$